

Total No. of Printed Pages—7

**4 SEM TDC PHYH (CBCS) C 10**

**2 0 2 2**

( June/July )

**PHYSICS**

( Core )

Paper : C-10

**( Analog Systems and Applications )**

Full Marks : 53

Pass Marks : 21

Time : 3 hours

*The figures in the margin indicate full marks  
for the questions*

1. Choose the correct answer : 1×5=5

(a) When reverse bias is applied to a junction diode

(i) width of depletion layer decreases

(ii) potential barrier increases

(iii) potential barrier decreases

(iv) minority carrier increases

( 2 )

- (b) The rectification efficiency of full-wave rectifier is \_\_\_\_\_ of half-wave rectifier.
- (i) equal
  - (ii) half
  - (iii) double
  - (iv) 1.21 times
- (c) Quiescence is a state of
- (i) activity
  - (ii) inactivity
  - (iii) amplification
  - (iv) switching
- (d) In a transistor amplifier, the input impedance should be
- (i) low
  - (ii) high
  - (iii) negligible
  - (iv) None of the above

22P/1270

( Continued )

( 3 )

- (e) Which of the following electrical characteristics is not exhibited by an ideal OP-AMP?
- (i) Infinite voltage gain
  - (ii) Infinite bandwidth
  - (iii) Infinite output resistance
  - (iv) Infinite slew rate
2. (a) Explain how depletion layer is formed under unbiased situation of a  $p-n$  junction diode. 3
- (b) Explain the current flow mechanism in forward and reverse biased  $p-n$  junction diode. 4
- Or
- Define the mobility of charge carriers and conductivity. Obtain an expression for the electrical conductivity of an intrinsic semiconductor. 1+3=4

22P/1270

( Turn Over )

( 4 )

3. (a) Explain with circuit diagram, the Zener diode as a voltage regulator. 3

(b) Describe the working of LED. 2

4. (a) Draw the C-E circuit of a transistor. Sketch its output characteristics. Explain the active, cut-off and saturation regions. 1+1+2=4

(b) Define  $\alpha$  and  $\beta$  of a transistor. Write the relation between them. 2

5. (a) Draw a voltage-divider bias circuit and derive an expression for its stability factor. 4

Or

A germanium transistor with  $\beta = 100$  is to be operated as a C-E amplifier with fixed bias method. The transistor operates at the signal collector current  $I_C = 1 \text{ mA}$  and  $V_{CE} = 4 \text{ V}$ . If a load resistance of  $2 \text{ k}\Omega$  is connected in the collector circuit, then find the base resistance to be connected. (For germanium transistor  $V_{BE} = 0.3 \text{ V}$ )

( 5 )

(b) Draw the small signal hybrid equivalent circuit of a common-emitter transistor amplifier and derive the expressions for current gain and input impedance. 4

Or

Explain class A, class B and class C amplifiers with graphical representation.

6. Draw and discuss the frequency response curve of an R-C coupled transistor amplifier showing cut-off frequencies and the bandwidth. 3

7. Discuss the effect of negative feedback on the input and output impedances of an amplifier. 3


8. State Barkhausen's criterion and explain the conditions that must be satisfied for feedback amplifier to produce steady oscillations. 1+2=3

( 6 )

Or

Draw circuit diagram of an R-C phase shift oscillator and explain its operation. 3

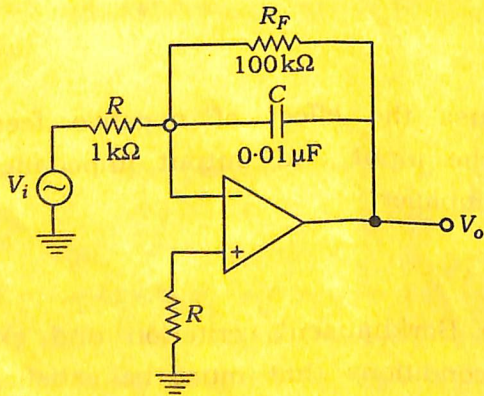9. (a) What is an OP-AMP? Draw the schematic block diagram of basic OP-AMP. 1+2=3
- (b) Explain with circuit diagram, the adder and subtractor using OP-AMP. 4
- (c) Determine the lower frequency limit (critical frequency) for the integrator circuit shown below : 3



Or

Discuss OP-AMP as log amplifier.

22P/1270

( Continued )

( 7 )

10. Draw the block diagram of successive approximation type A/D converter. 3

Or

Draw the circuit diagram of weighted resistor type D/A converter.

\*\*\*

22P-5000/1270

4 SEM TDC PHYH (CBCS) C 10